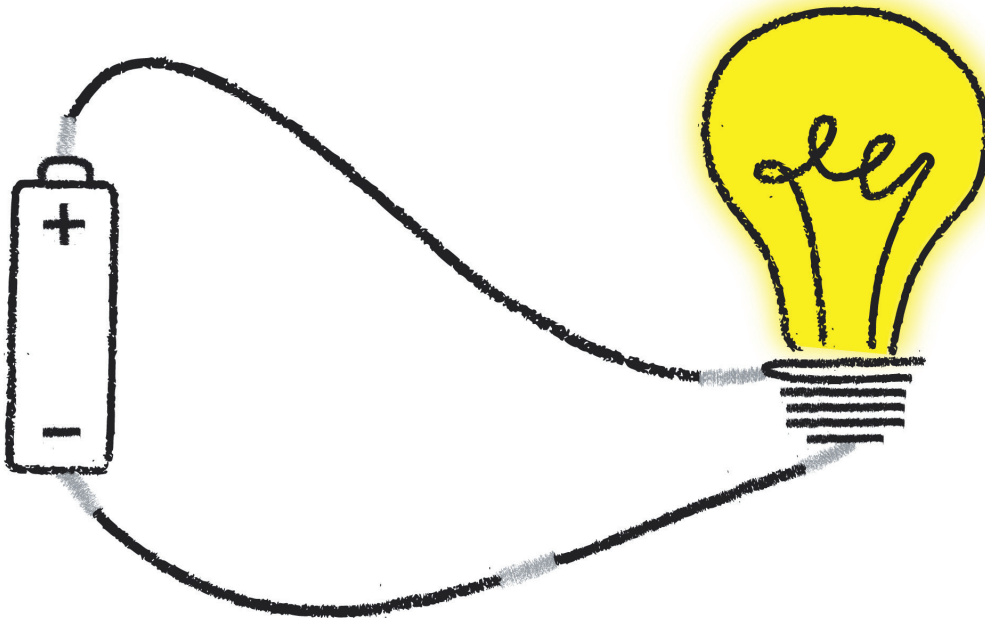


Name _____

Circuits – Answer Key

Directions: Use the Word Bank to answer the questions about the circuit.



Word Bank

Open

Conductors

Output device

Light

Chemical

Power source

Closed

1. The wires used in this circuit are Conductors.
2. The battery works as the Power source of this circuit.
3. This is an example of a(n) Closed circuit.
4. The light bulb is the Output device in this circuit.
5. Name a form of energy demonstrated by the lit bulb: Light.