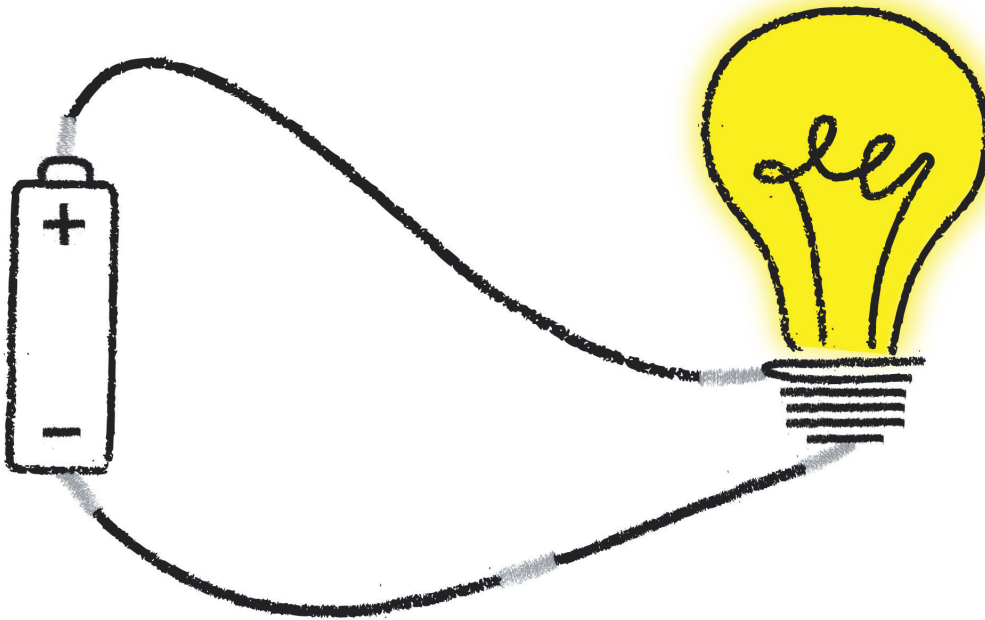


Name _____

Circuits

Directions: Use the Word Bank to answer the questions about the circuit.



Word Bank

Open

Conductors

Output device

Light

Chemical

Power source

Closed

1. The wires used in this circuit are _____.
2. The battery works as the _____ of this circuit.
3. This is an example of a(n) _____ circuit.
4. The light bulb is the _____ in this circuit.
5. Name a form of energy demonstrated by the lit bulb: _____.